

Instructable

Step 1: materials

1. Order the listed items in the bill of materials, the optional price is in case this is your first project with no prior components.

Step 2: Preparing the Power Distribution Board

1. Create the Power Distribution Point:

- Use a copper print plate to create a power distribution point for the 5V output from the L298N.
- Solder three wire terminals for the 5V line and three for the ground line onto the print plate.
- Ensure that each terminal is securely soldered to avoid loose connections during operation.

2. Connecting to the Motor Driver:

- Attach the 5V terminals to the 5V output of the L298N module.
- Connect the ground terminals to the GND pin of the L298N.

Step 3: Wiring the Motors

1. Solder the Wires to the Motors:

- Solder the wires from the L298N module to the DC micro metal gear motors. Attach OUT1 and OUT2 to one motor and OUT3 and OUT4 to the other.
- Test the motor connections to ensure proper rotation direction and functionality.

2. Mounting the Motors:

- Attach the motor brackets to the robot platform.
- Drill holes on the left and right sides of the platform for mounting the motor brackets.
- Secure the motors onto the platform using screws.

Step 4: Mounting the Components on the Platform

1. Glue the Battery Holders and Switch:

- Position the battery holders and the switch on the robot platform where they won't obstruct other components.
- Use hot glue or epoxy to secure them in place.

2. Mount the Arduino, L298N, Boost Converter, and HC-05:

- Glue the Arduino, L298N motor driver, boost converter, and HC-05 Bluetooth module onto the platform. Make sure they are spaced well for easy wiring.

3. Install the QTR-8A Sensor Array:

- Glue the QTR-8A sensor array at the front of the platform with the sensors pointing down towards the ground.
- Drill four holes at the front of the platform near the sensor array to attach the ball rollers.

Step 5: Electrical Connections

1. Power Wiring:

- **Switch to Boost Converter:**
 - Solder the positive wire from the battery pack to one terminal of the switch.
 - Solder a wire from the other terminal of the switch to the positive input of the boost converter.
- **Battery to Boost Converter:**
 - Connect the negative wire from the battery pack to the negative input of the boost converter.
- **Boost converter calibration:**
 - Measure the output of the converter with a multimeter and turn the potentiometer until you reach 12V.
- **Boost Converter to L298N:**
 - Connect the positive output of the boost converter to the 12V input of the L298N module.
 - Connect the negative output of the boost converter to the ground terminals.

2. Arduino and Sensor Connections:

- **Grounding:**
 - Connect a wire from the common ground terminal to the GND pin of the L298N.
 - From the common 5V terminal, connect a wire to the Arduino's 5V pin and another to the VCC input of the HC-05 Bluetooth module.
- **Sensor Power:**
 - From the Arduino, connect the 5V pin to the VCC input on the QTR-8A sensor array.
 - Connect the Arduino's GND pin to the GND pin on the QTR-8A sensor array.

3. Signal Wiring:

- **HC-05 Bluetooth Module:**
 - Solder a voltage divider with 1k Ω and 2k Ω resistors onto a print plate.
 - Connect the RX pin from the HC-05 to the input of the voltage divider.

- The 2k Ω side of the divider goes to GND, and the 1k Ω side goes to the TX port of the Arduino.
- **Motor Driver Control:**
 - Connect Arduino digital pins 4 and 5 to IN1 and IN2 of the L298N, respectively.
 - Connect digital pins 7 and 8 to IN3 and IN4 of the L298N.
 - Connect pins 9 and 10 to ENA and ENB to control motor speed via PWM.

4. **Sensor Array Wiring:**

- Attach jumper wires from the QTR-8A sensor array to the analog inputs A0 to A5 on the Arduino.

Step 6: Final Assembly and Testing

1. **Check Connections:**

- Review all connections to ensure proper placement and secure soldering. Verify that no wires are crossing or shorting.

2. **Power On and Test:**

- Insert batteries into the holders and switch on the power.
- Use a multimeter to check for correct voltage levels at various points in the circuit.
- Program the Arduino with a basic code to test motor operation, sensor readings, and Bluetooth communication.

3. **Fine-Tuning:**

- If the motors are not turning in the desired direction, reverse the wiring on the L298N outputs.
- Adjust the sensor array position for optimal line detection.

4. **Programming:**

- With a micro-usb you can connect to the Arduino IDE and program to the Arduino leonardo



